

SWBAT: calculate electrical power

Jan 4-7:20 AM

Welcome!!!

H. Leslie Grebe


SECA Physics
Friday 11 March 2016

- * Pick up:
- slip of paper (for later)
- yellow concept sheet

Opening Questions:

Is this a series or parallel circuit? How much total resistance would you guess there is?

MORE THAN
ONE PATH

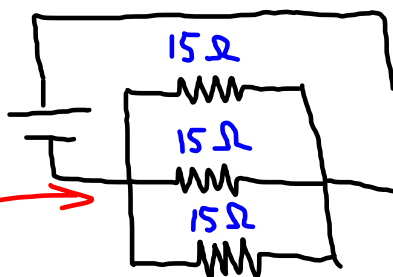

$$R_T = \frac{15\Omega}{3} = 5\Omega$$

Reminder
Centering

Sep 7-7:04 AM



Mystery Resistor - extra credit

- You may work alone or with at most one other person of your choosing.
- Get a "Mystery Resistor" labeled with a letter from Leslie
- Use the same equipment that our teams used in class. Take measurements that will allow you to calculate the resistance (in Ohms) of your resistor.
- You may work when there is spare time in class or arrange other time with Leslie.

Due by 3:00 Friday 3/18

Jan 19-7:12 AM

Concept Sheet -- get yours out

We'll fill in a concept & "bike analogy" column today

5 or 6 rows

Concept	Meaning	Sym- bol	Units	Bike Analogy	WATER ANALOGY
CHARGE	PROPERTY OF PROTONS & ELECTRONS THAT CAUSES ATTRACTION & REPULSION	q	COULOMBS C		WATER ITSELF
VOLTAGE = ELECTRIC POTENTIAL	POTENTIAL BASED ON POSITION IN AN ELECTRIC FIELD. "PUSH"	V	VOLTS V $V = I \cdot R$	- PERSON - PEDALING \Rightarrow THE PUSH	- PUMP - PRESSURE \Rightarrow PUSH!
CURRENT	THE FLOW OF ELECTRIC CHARGE. = CHARGE TIME	I	AMPERES $A = \frac{C}{s}$	CHAINS, WHEEL, BIKE MOVING	FLOW OF WATER
RESISTANCE	OPPOSITION OF CURRENT (AGAINST THE FLOW)	R	OHMS Ω	BRAKES	
OHM'S LAW	VOLTAGE = CURRENT X RESISTANCE	$V = I \cdot R$	$1V = 1A \cdot 1\Omega$		
POWER	AMOUNT OF WORK DONE PER SECOND POWER = CURRENT X VOLTAGE	$P = I \cdot V$	WATTS W		

Extend Page


$$1W = 1V \cdot 1A$$

$$= \frac{J}{s}$$

Feb 23-7:34 AM

Power in Circuits:

$$\text{POWER} = \text{CURRENT} \times \text{VOLTAGE}$$

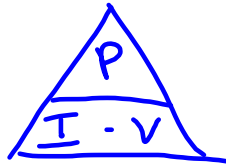

cpcd34-2

a) How much power is needed to produce 3A using 12V?

$$P = I \cdot V = 3A \cdot 12V = 36W$$

b) How much current will result from 10 V and 60 W of power?

$$I = \frac{P}{V} = \frac{60W}{10V} = 6A$$

c) How many volts produce 10 A of current to make 5 W of power?

$$V = \frac{P}{I} = \frac{5W}{10A} = 0.5V$$

Mar 21-7:21 AM

Daily 3 Questions

- * Every day except test/project days
- * 3 Questions on the topics of the day
- * Main source of daily points
- * I am happy to give credit when I have no concerns about someone giving or getting help with the answers.

You can't get your points if you don't have your **NAME!!!**

Name	Period
1.	
2.	
3.	

Sep 9-7:32 AM

1) What does "I" stand for in a formula?

CURRENT

2) What is the **power** when a voltage of 120 V drives a 2A current through a device?

240W

3) How much current will result from 10 V and 60 W of power?

$$I = \frac{P}{V} = \frac{60W}{10V} = 6A$$

Feb 18-6:59 AM


1) Which bulb will be brightest?

A.

B.

C.

All the same.

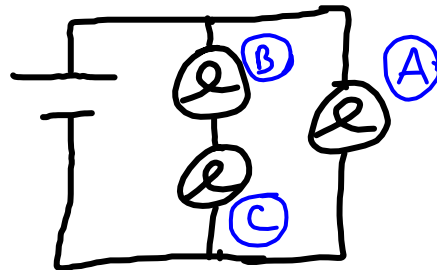

2) What is the **power** when a voltage of 120 V drives a 2A current through a device?

3) How much current will result from 10 V and 60 W of power?

Feb 18-6:59 AM